

# Worksheet: Circuits with Inductors and Capacitors in Series



**Q1:** An  $LC$  circuit in an AM tuner (in a car stereo) uses a coil with an inductance of 2.5 mH and a variable capacitor. If the natural frequency of the circuit is to be adjustable over the range 540 to 1 600 kHz (the AM broadcast band), what range of capacitance is required?



Question Video

A  $3.0 \times 10^{-11}$  F to  $4.5 \times 10^{-12}$  F

B  $3.4 \times 10^{-11}$  F to  $4.0 \times 10^{-11}$  F

C  $3.5 \times 10^{-11}$  F to  $4.0 \times 10^{-12}$  F

D  $3.3 \times 10^{-11}$  F to  $5.0 \times 10^{-12}$  F

E  $3.5 \times 10^{-11}$  F to  $4.4 \times 10^{-12}$  F

**Q2:** The self-inductance of an  $LC$  circuit is 0.20 mH. The circuit's capacitance is 5.0 pF. What is the angular frequency of the current in the circuit?

A  $3.2 \times 10^{-7}$  rad/s

B  $4.6 \times 10^{-7}$  rad/s

C  $5.1 \times 10^{-7}$  rad/s

D  $2.6 \times 10^{-7}$  rad/s

E  $3.8 \times 10^{-7}$  rad/s

**Q3:** In an oscillating  $LC$  circuit, the maximum charge on the capacitor is  $2.0 \times 10^{-6}$  C and the maximum current through the inductor is 8.0 mA.

► What is the period of the oscillations?

A  $7.9 \times 10^{-4} \text{ s}$

B  $9.2 \times 10^{-4} \text{ s}$

C  $8.6 \times 10^{-4} \text{ s}$

D  $7.3 \times 10^{-4} \text{ s}$

E  $6.8 \times 10^{-4} \text{ s}$

► How much time elapses between an instant when the capacitor is uncharged and the next instant when it is fully charged?

A  $4.0 \times 10^{-4} \text{ s}$

B  $9.2 \times 10^{-4} \text{ s}$

C  $7.0 \times 10^{-4} \text{ s}$

D  $5.8 \times 10^{-4} \text{ s}$

E  $2.5 \times 10^{-4} \text{ s}$

**Q4:** When a camera uses a flash, a fully charged capacitor discharges through an inductor. In what time must the 0.200 amperes current through a 5.00 mH inductor be switched on or off to induce a 700 V emf?

A 32.1  $\mu\text{s}$

B 98.7  $\mu\text{s}$

C 1.43  $\mu\text{s}$

D 17.3  $\mu\text{s}$

E 14.1  $\mu\text{s}$

**Q5:** What is the self-inductance of an LC circuit that oscillates at 90 Hz when the capacitance is 30  $\mu\text{F}$ ?

A 0.20 H

B 0.10 H

C 0.45 H

D 9.1 H

E 4.1 H

**Q6:** The self-inductance and capacitance of an oscillating LC circuit are  $L = 50 \text{ mH}$  and  $C = 4.0 \mu\text{F}$  respectively.

► What is the frequency of the oscillations?

A 120 Hz

B 210 Hz

C 560 Hz

D 360 Hz

E 360 Hz

► If the maximum potential difference between the plates of the capacitor is 60 V, what is the maximum current in the circuit?

A 0.36 A


B 1.3 A

C 1.9 A

D 0.54 A

E 12 A

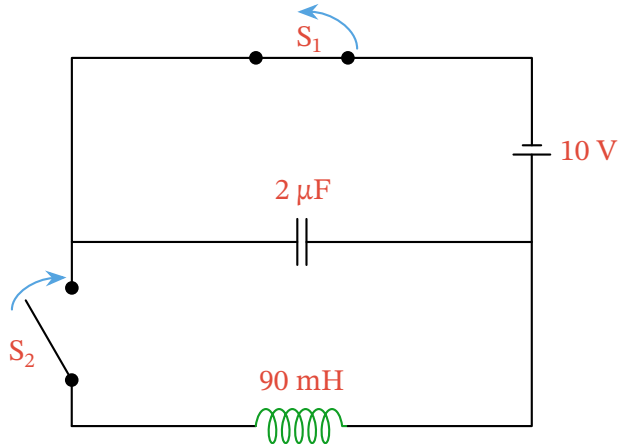**Q7:** In the circuit shown,  $S_1$  is opened and  $S_2$  is closed simultaneously, resulting in a circuit that consists of just an inductor and a capacitor.



► Determine the frequency of the resulting oscillations.

- A 66 Hz
- B 380 Hz
- C 90 Hz
- D 980 Hz
- E 360 Hz

► Determine the maximum charge on the capacitor.

A  $69 \mu\text{C}$

B  $20 \mu\text{C}$

C  $150 \mu\text{C}$

D  $120 \mu\text{C}$

E  $63 \mu\text{C}$

► Determine the maximum current through the inductor.

A  $77 \times 10^{-3} \text{ A}$

B  $47 \times 10^{-3} \text{ A}$

C  $98 \times 10^{-3} \text{ A}$

D  $88 \times 10^{-3} \text{ A}$

E  $69 \times 10^{-3} \text{ A}$

► Determine the electromagnetic energy of the oscillating circuit.

A  $98 \mu\text{J}$


B  $100 \mu\text{J}$

C  $12 \mu\text{J}$


D  $30 \mu\text{J}$

E  $96 \mu\text{J}$

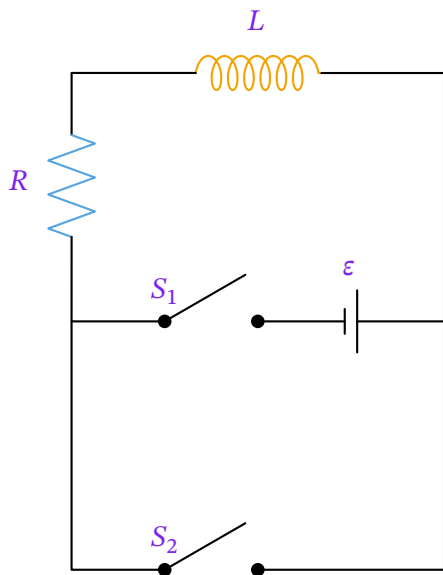**Q8:** Part (a) of the diagram shows an  $RL$  circuit consisting of a resistor, an inductor, and a constant source of emf.  $S_1$  and  $S_2$  are switches. When  $S_1$  is closed, the circuit is equivalent to the single-loop circuit shown in part (b) of the diagram. The value of the emf,  $\epsilon$ , is equal to 18 V; the self-inductance,  $L$ , of the inductor is 30 mH; and the resistor has a resistance of  $8.0 \Omega$ .



(a)

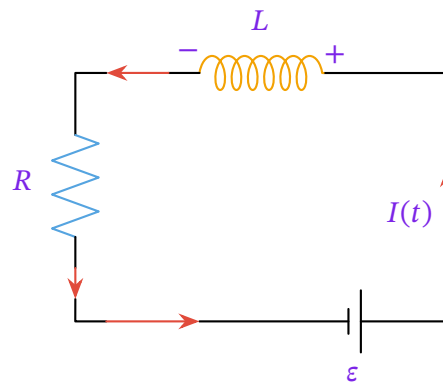

(b)

► Determine the inductive time constant of the circuit.

- A  $0.21 \times 10^{-3} \text{ s}$
- B  $3.8 \times 10^{-3} \text{ s}$
- C  $3.0 \times 10^{-3} \text{ s}$
- D  $12 \times 10^{-3} \text{ s}$
- E  $5.8 \times 10^{-3} \text{ s}$

► Determine the initial current through the resistor.

A 12 A

B 0.0 A

C 5.6 A

D 1.2 A

E 3.0 A

► Determine the final current through the inductor.

A 4.0 A

B 2.3 A

C 2.6 A

D 4.3 A

E 12 A

► Determine the current through the resistor when  $t = 2\tau_L$ .

A 7.8 A

B 2.0 A

C 3.2 A

D 4.0 A

E 0.36 A



► Determine the voltage across the inductor when  $t = 3\tau_L$ .

A 0.81 V

B 0.90 V

C 9.6 V

D 6.2 V

E 0.15 V